



**COMP: 106**

**LOGIC DESIGN**

**2023 PROJECT ASSIGNMENT**



# TEAM #18

- 1) MOHAMED HESHAM MOHAMED
- 2) MOHAMED YASSER MOHAMED
- 3) ALI MAGDY ABO EL-MAHASAN
- 4) MAHMOUD YOUSSEF RASLAN
- 5) AMR KHALED ISMAIL

Special thanks to Dr. Naglaa M. Reda

**Q:** Design the code converter that accepts the BCD code of a decimal digit and outputs its equivalent 8, 4, 2, 1, augmented with negative sign bit.

**Step 1:** There are 4 inputs A, B, C, D, and 5 outputs w, x, y, z, s.

**Step 2:** The truth table is 

**Step 3:** Boolean functions

$$w = \sum(8, 9)$$

$$x = \sum(4, 5, 6, 7)$$

$$y = \sum(2, 3, 6, 7)$$

$$z = \sum(1, 3, 5, 7, 9)$$

$$s = \sum(1, 2, 3, 4, 5, 6, 7, 8, 9)$$

Input BCD				Output 8,4,2,1				Sign
A	B	C	D	w	x	y	z	s
0	0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1	1
0	0	1	0	0	0	1	0	1
0	0	1	1	0	0	1	1	1
0	1	0	0	0	1	0	0	1
0	1	0	1	0	1	0	1	1
0	1	1	0	0	1	1	0	1
0	1	1	1	0	1	1	1	1
1	0	0	0	1	0	0	0	1
1	0	0	1	1	0	0	1	1

## Step 4: Simplified boolean functions

$w=A$

		$CD$		$C$	
		00	01	11	10
$AB$	00	$m_0$	$m_1$	$m_3$	$m_2$
	01	$m_4$	$m_5$	$m_7$	$m_6$
	11	$m_{12}$ <b>X</b>	$m_{13}$ <b>X</b>	$m_{15}$ <b>X</b>	$m_{14}$ <b>X</b>
	10	$m_8$ <b>1</b>	$m_9$ <b>1</b>	$m_{11}$ <b>X</b>	$m_{10}$ <b>X</b>

$A$   $B$   $D$

$x=B$

		$CD$		$C$	
		00	01	11	10
$AB$	00	$m_0$	$m_1$	$m_3$	$m_2$
	01	$m_4$ <b>1</b>	$m_5$ <b>1</b>	$m_7$ <b>1</b>	$m_6$ <b>1</b>
	11	$m_{12}$ <b>X</b>	$m_{13}$ <b>X</b>	$m_{15}$ <b>X</b>	$m_{14}$ <b>X</b>
	10	$m_8$	$m_9$	$m_{11}$ <b>X</b>	$m_{10}$ <b>X</b>

$A$   $B$   $D$



$$y=C$$

		$CD$		$C$	
		00	01	11	10
$AB$	00	$m_0$	$m_1$	$m_3$ 1	$m_2$ 1
	01	$m_4$	$m_5$	$m_7$ 1	$m_6$ 1
	11	$m_{12}$ X	$m_{13}$ X	$m_{15}$ X	$m_{14}$ X
	10	$m_8$	$m_9$	$m_{11}$ X	$m_{10}$ X

$D$

$B$

$$z=D$$

		$CD$		$C$	
		00	01	11	10
$AB$	00	$m_0$	$m_1$ 1	$m_3$ 1	$m_2$
	01	$m_4$	$m_5$ 1	$m_7$ 1	$m_6$
	11	$m_{12}$ X	$m_{13}$ X	$m_{15}$ X	$m_{14}$ X
	10	$m_8$	$m_9$ 1	$m_{11}$ X	$m_{10}$ X

$D$

$B$


$$s=A+B+C+D$$

		$CD$		$C$	
		00	01	11	10
$AB$	00	$m_0$	$m_1$ 1	$m_3$ 1	$m_2$ 1
	01	$m_4$ 1	$m_5$ 1	$m_7$ 1	$m_6$ 1
	11	$m_{12}$ X	$m_{13}$ X	$m_{15}$ X	$m_{14}$ X
	10	$m_8$ 1	$m_9$ 1	$m_{11}$ X	$m_{10}$ X


$D$

$B$

**Step 5: The logic diagram is**

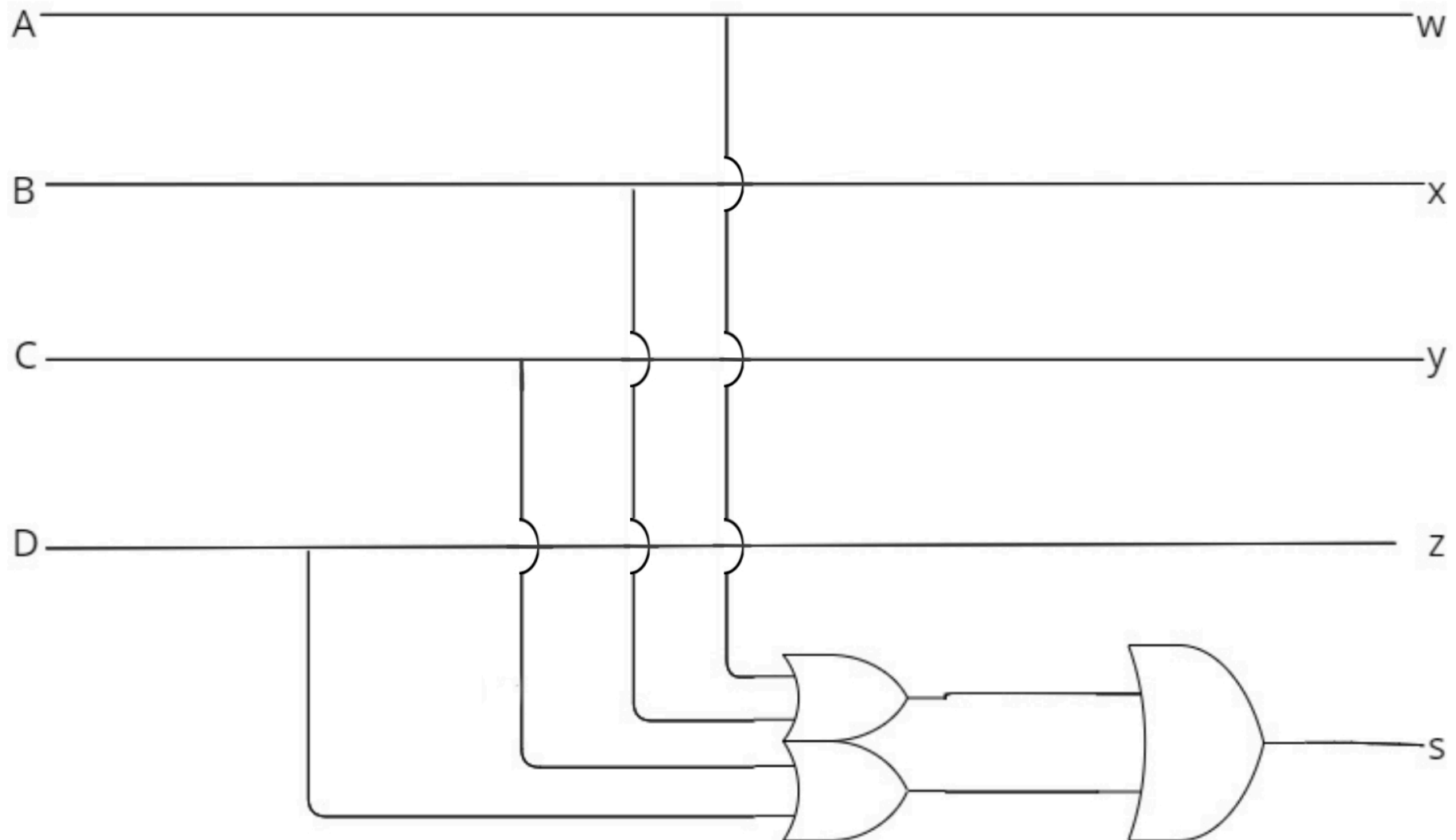

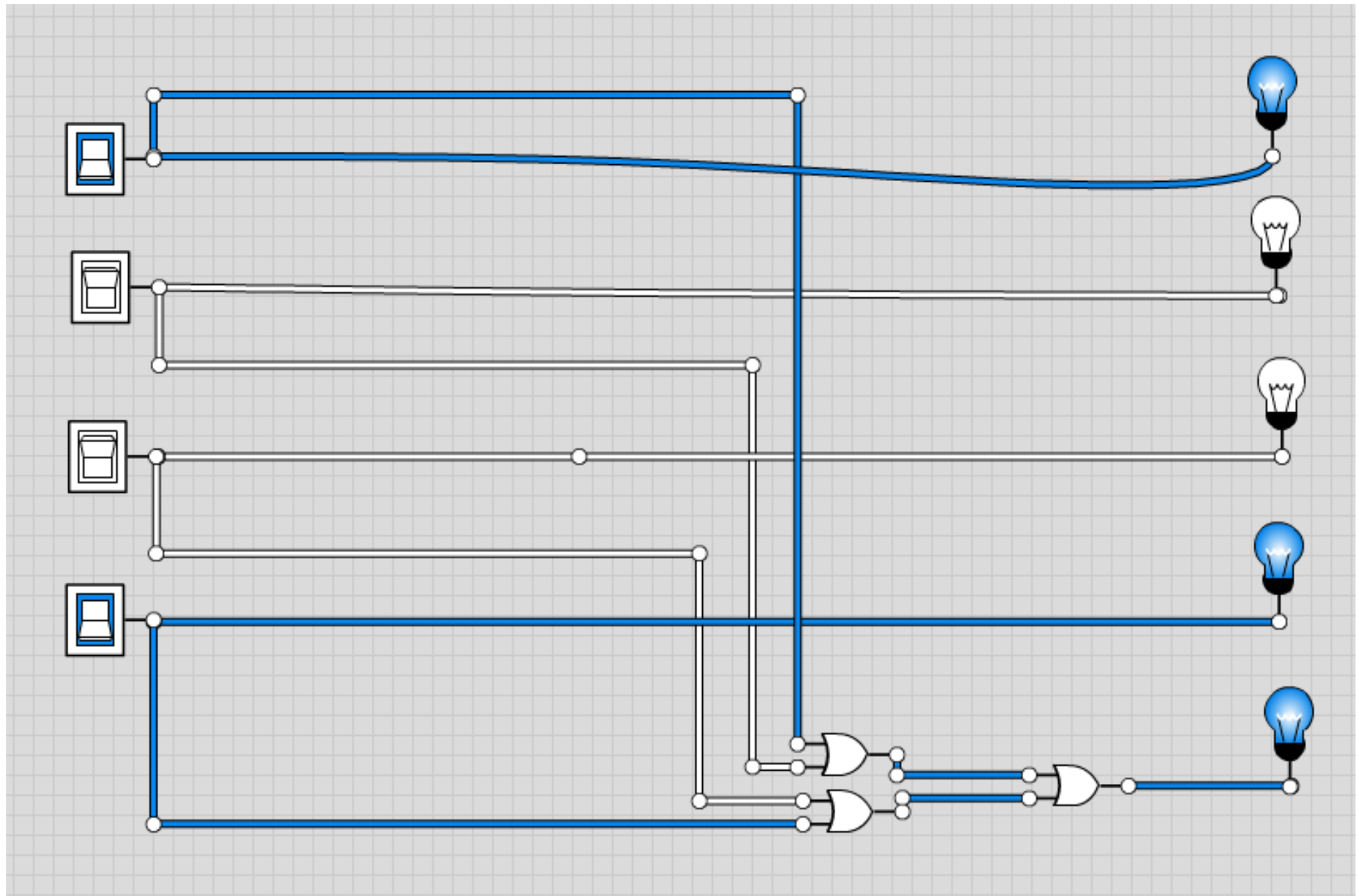***Step 6: The simulator for design is***



T H A N K  
Y O U